

# Dynamic Offset-Cancellation Techniques

Kofi Makinwa

Electronic Instrumentation Laboratory, DIMES  
Delft University of Technology  
Delft, The Netherlands



# Motivation

- Many sensors (e.g. thermopiles, bridges, hall sensors) output DC signals in the millivolt range
- These signals are best processed on-chip
- However, the offset of basic IC amplifiers is **also** in the millivolt range, especially in CMOS
- Therefore, special techniques are required to reduce the offset of IC amplifiers

# Outline


- Differential amplifiers
  - Offset and  $1/f$  noise
- Trimming
- Dynamic Offset Cancellation
  - Auto-zeroing
  - Chopping
- Interfacing Examples
- Conclusion
- References

# Differential Amplifiers

Differential amplifiers are widely used to amplify DC signals

Balanced structure is

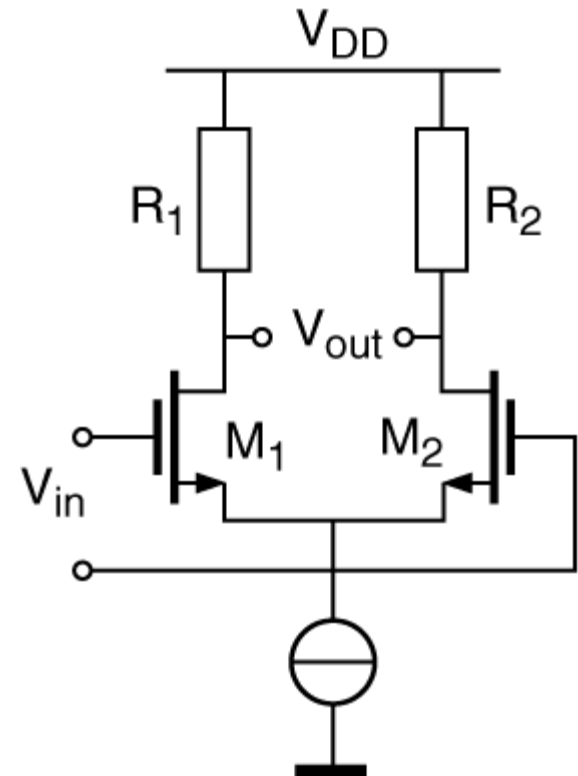- Nominally offset free
- Rejects common-mode and power supply interference
- Easily realized in both CMOS and bipolar technologies



# Offset in Differential Amplifiers

Component mismatch  $\Rightarrow$  **offset**

e.g.  $R_1 \neq R_2$ ,  $M_1 \neq M_2$


Mismatch is mainly due to

- Process variation
- Lithographic errors

All other things being equal:

Bipolar  $\Rightarrow V_{os} \sim 0.1\text{mV}$

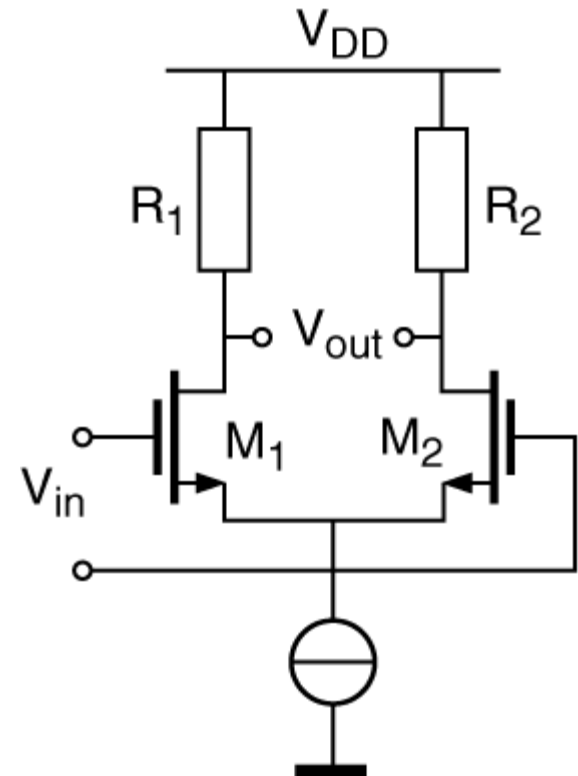CMOS  $\Rightarrow 10 - 100$  times worse!



# Drift and Noise

## Drift

- Temperature, ageing and packaging stress cause time-varying offset
- Trimming bipolar DA's reduces **both** offset and temperature drift [1]. Not true of MOSFETs!


## $1/f$ (or flicker) noise

- MOSFETs are worse than bipolar transistors
- Varies inversely with transistor area
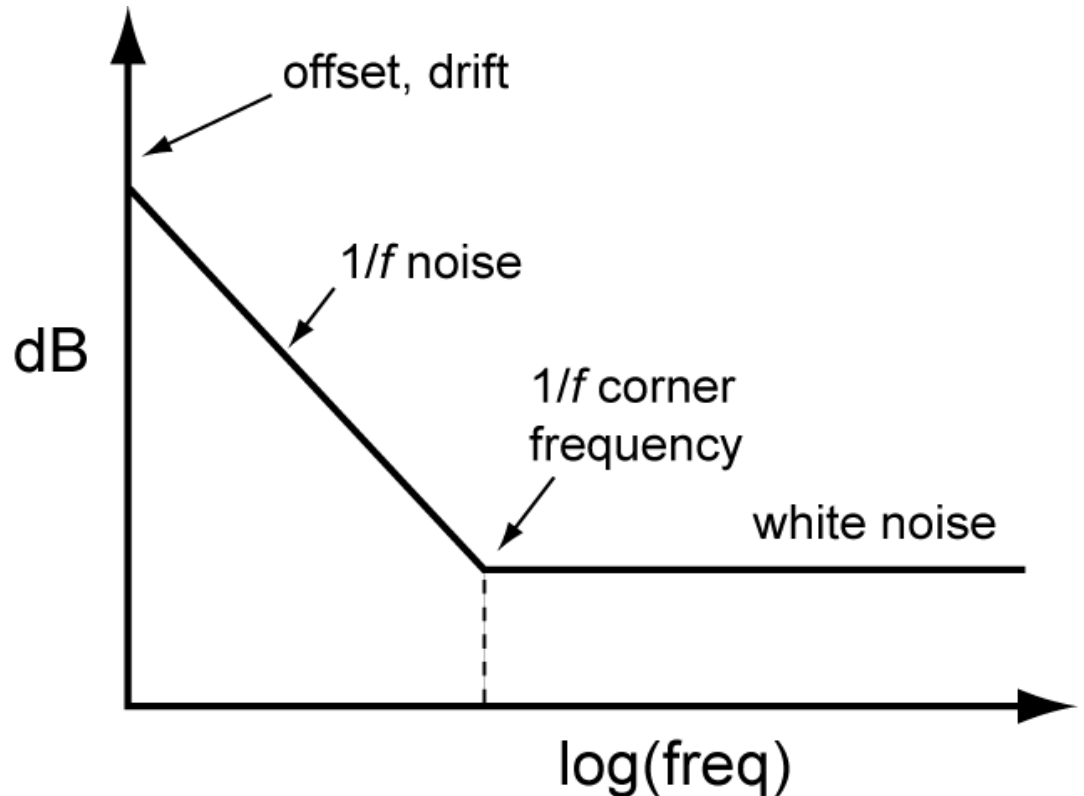
# Amplifier Behaviour Near DC

Characterized by

- Offset
- Drift
- $1/f$  noise
- PSRR, CMRR



# What to Do?

Offsets and  $1/f$  noise are part of life

But we can reduce offset “enough” by

1. Using “large” devices and good layout [2]
2. Trimming (bipolar) or by
3. Dynamic offset-cancellation (DOC) techniques

DOC techniques also reduce  $1/f$  noise!



# Trimming

External potentiometers

- Extra component and extra pins

In IC technology [3]

- Laser trimming
- Component switching
  - Zener zapping
  - Fusible links
  - PROM

Trimming  $\Rightarrow$  extra test infrastructure

# DOC Techniques

## **Auto-zeroing**

Sampled data

Sample offset,  
then subtract

## **Chopping**

Continuous time


Modulate offset  
away from DC

Switches required  $\Rightarrow$  CMOS or BiCMOS

# DOC Techniques Versus Trimming


- + reduction of offset and  $1/f$  noise
- + excellent long term stability
- + no additional costs for testing
  
- reduced bandwidth
- increased circuit complexity
- aliasing & intermodulation issues

# Auto-zero Principle

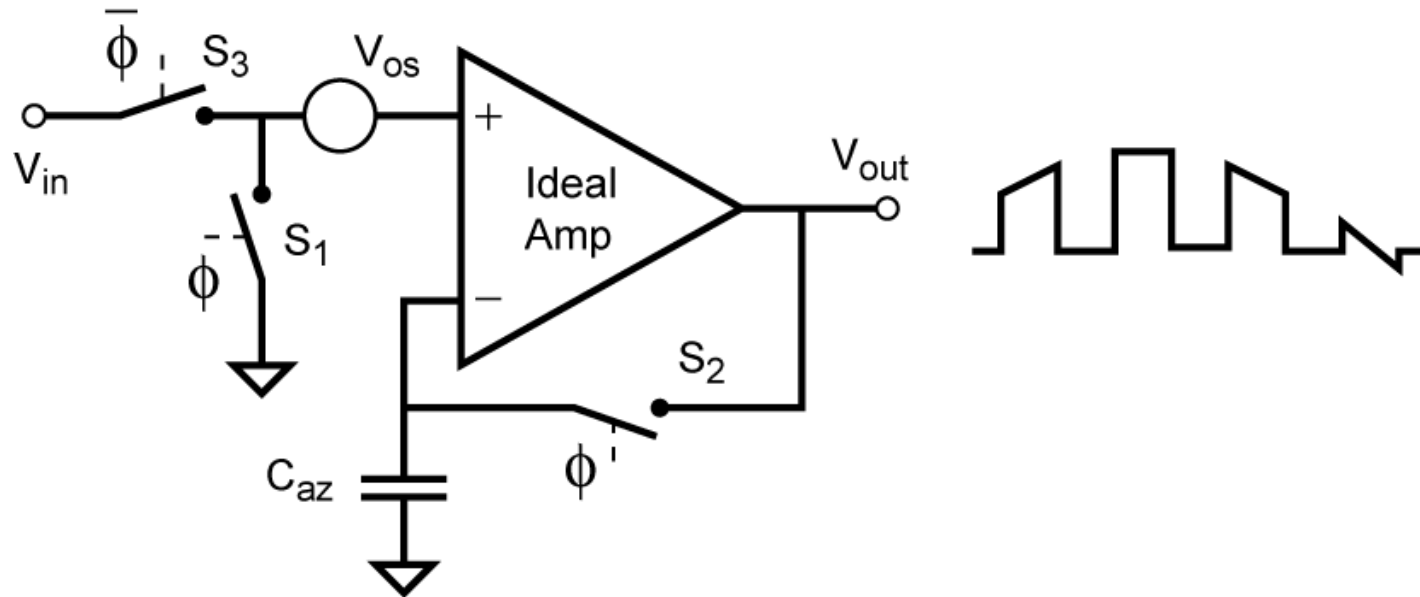

- $S_{1,2}$  closed  $\Rightarrow$  amplifier offset is stored on  $C_{az}$
- $S_3$  closed  $\Rightarrow$  output signal is available
- Residual offset  $\sim V_{os}/A$

# Charge Injection (1)

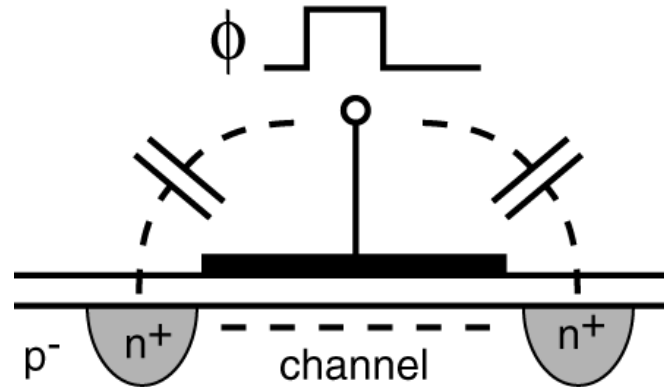


Occurs when MOSFETs switch **OFF**

Consists of two components

1. Channel charge,  $Q_{ch} = WLC_{ox}(V_{GS} - V_t)$
2. Overlap capacitance between the gate and the source/drain diffusions


# Charge Injection (2)

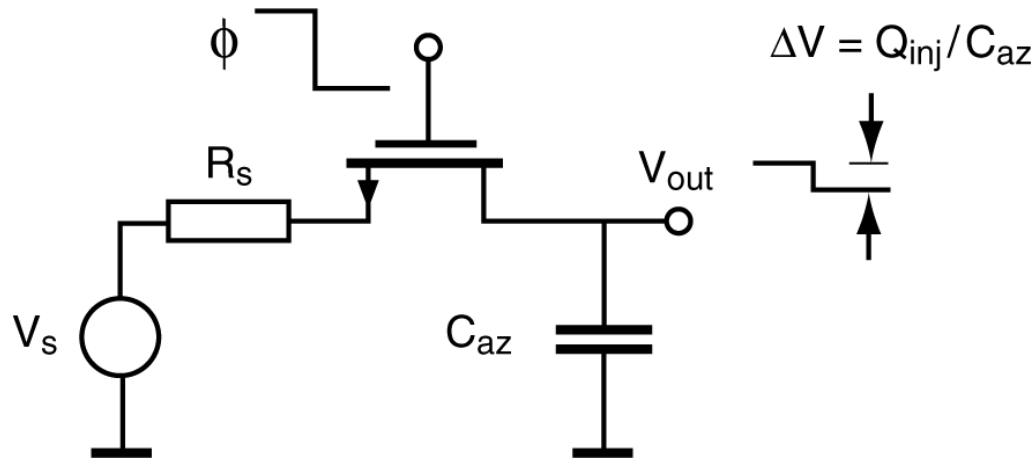

Error voltage depends on [4,5]


- Source impedance
- Transistor area (WL)
- Value of  $C_{az}$
- Clock amplitude & slew rate

# Switched Capacitor Amplifier (1)

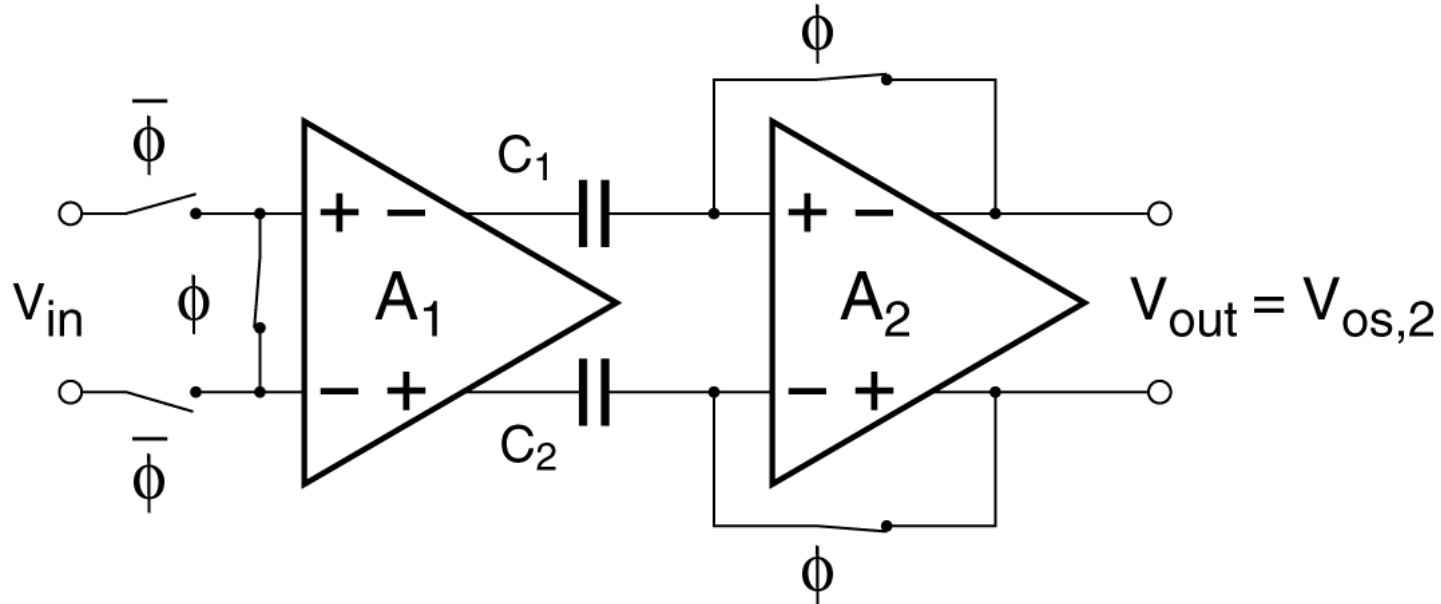

- During the auto-zero phase, the offset of  $A_1$  and  $A_2$  is stored on  $C_{1,2}$

# Switched Capacitor Amplifier (2)

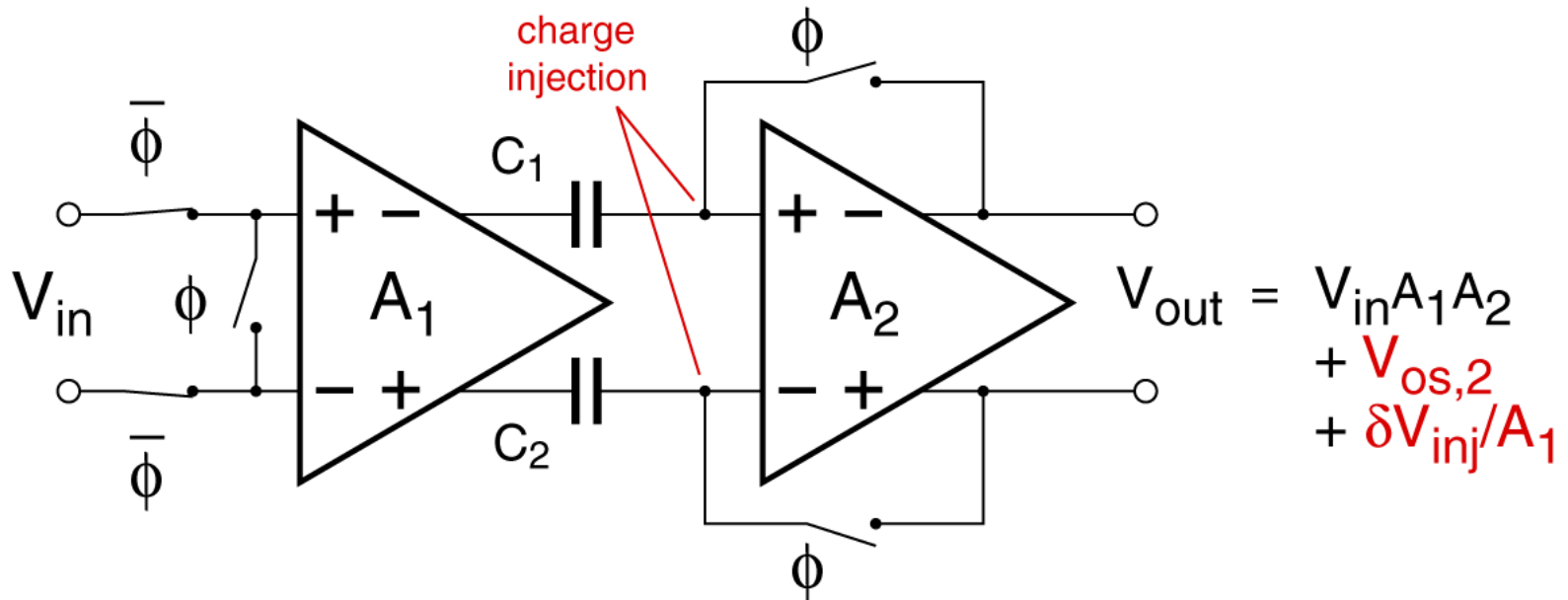

- During the next phase,  $V_{in}$  is amplified
- Differential topology  $\Rightarrow$  1<sup>st</sup> order cancellation of charge injection errors



# Residual Offset of Auto-zeroing

Determined by

- Charge injection
- Leakage on  $C_{az}$
- Limited amplifier gain & bandwidth ( $f_c$ )

In practice

- $C_{az}$  as large as possible (sometimes external)
- Multi-stage amplifier topologies
- $f_c \gg$  sampling frequency  $f_s$
- Residual offsets of 1-10 $\mu$ V

# Residual Noise of Auto-zeroing (1)


$$V_{n,az}(f) = V_n(f) * (1 - H(f))$$

$H(f)$  is the frequency response of the S&H


$$H(f) = \text{sinc}(f)$$

$\Rightarrow 1-H(f)$  is a HPF

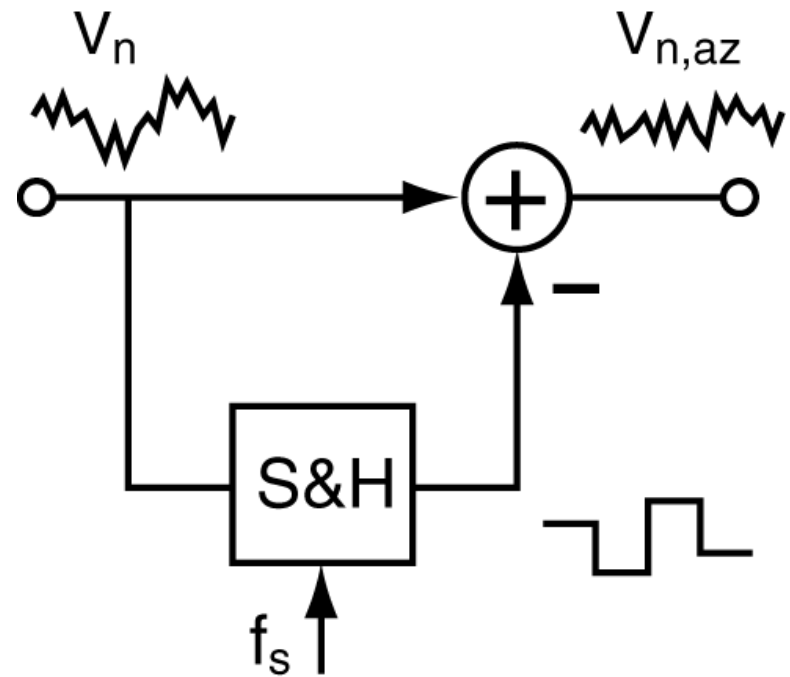$\Rightarrow$  Offset and  $1/f$  noise reduction!




# Residual Noise of Auto-zeroing (2)

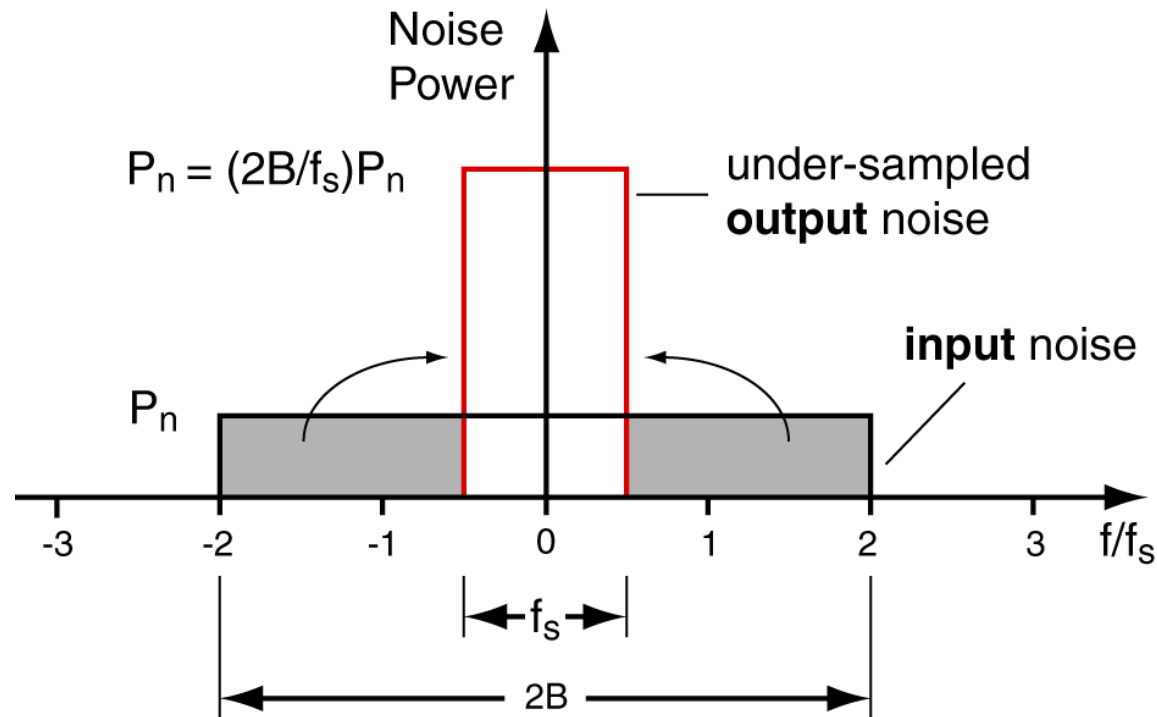


- Since noise bandwidth  $B > f_s \Rightarrow$  input noise is folded back to DC
- The result is LP filtered by the Hold function

# Residual Noise of Auto-zeroing (3)

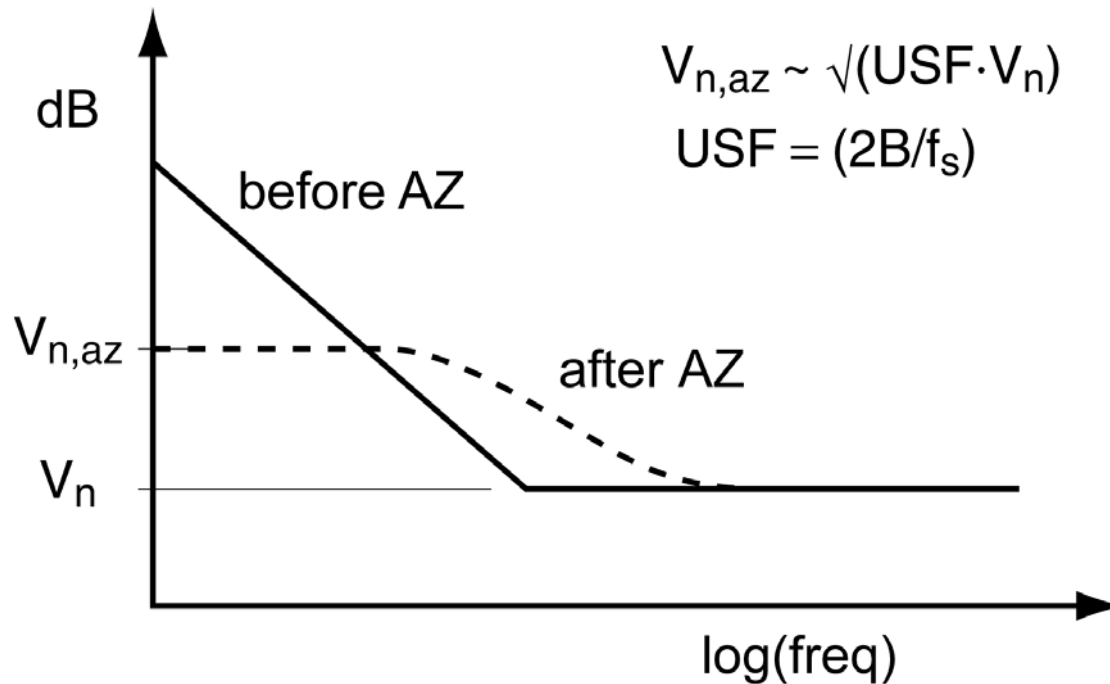


- $1/f$  noise is removed **but** noise foldover occurs [6]
- For a 1st order LPF,  $B = \pi f_c/2$
- State of the art is  $48\text{nV}/\sqrt{\text{Hz}}$  [7]

# Digital Trimming

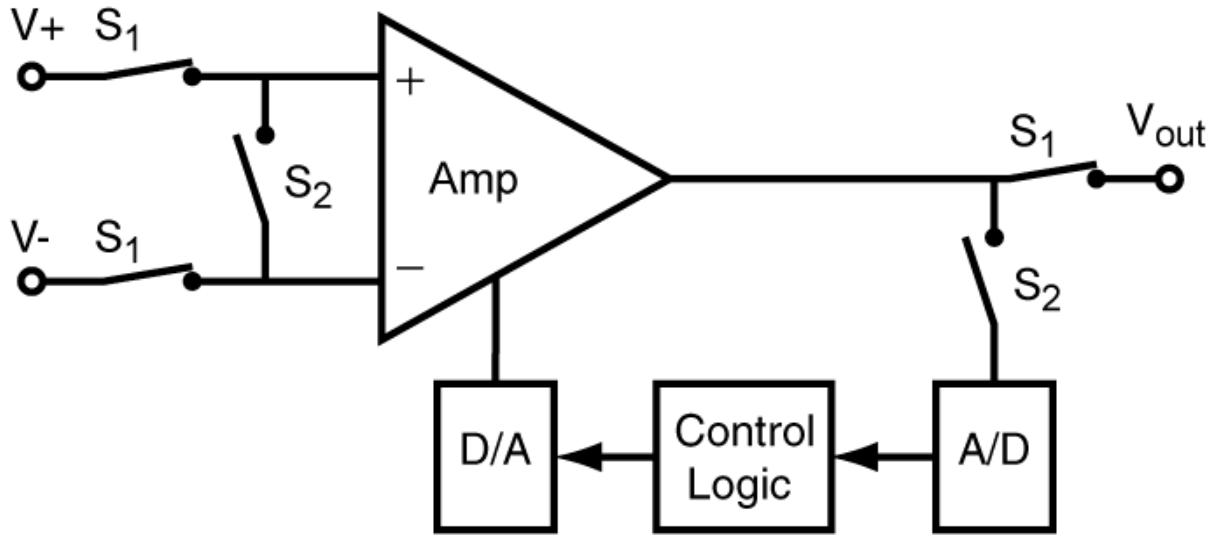

- Auto-zero at power on [8]
- No reduction of  $1/f$  noise
- But no bandwidth limitation
- Residual offset determined by D/A resolution

# The 3 Signal Method

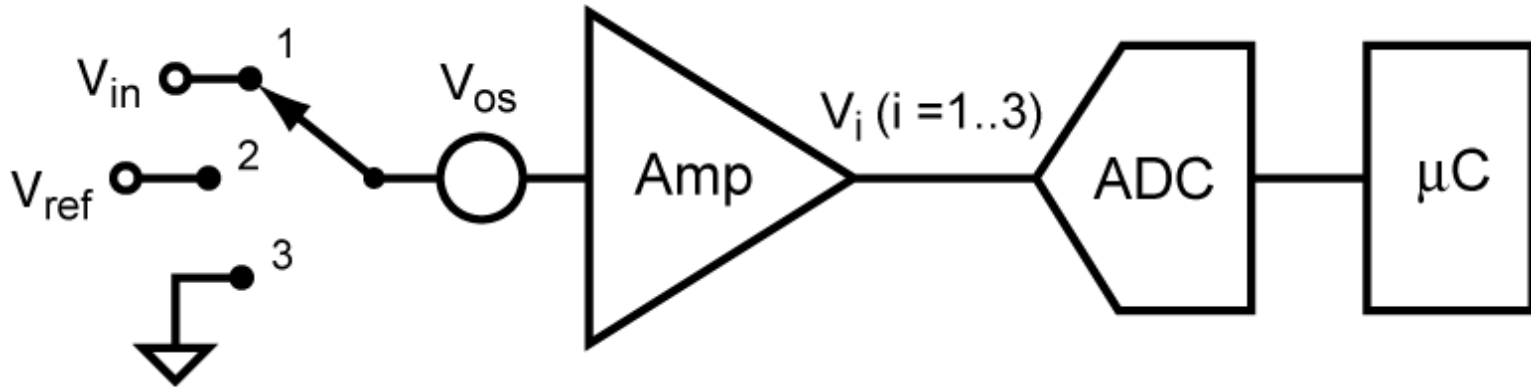

- Phase 1:  $V_1 = A(V_{os} + V_{in})$


- Phase 2:  $V_2 = A(V_{os} + V_{ref})$

- Phase 3:  $V_3 = AV_{os}$

$\Rightarrow A, V_{os}$  and  $V_{in}$  can be calculated

- Easy to implement if a  $\mu C$  is available


# Chopping Principle

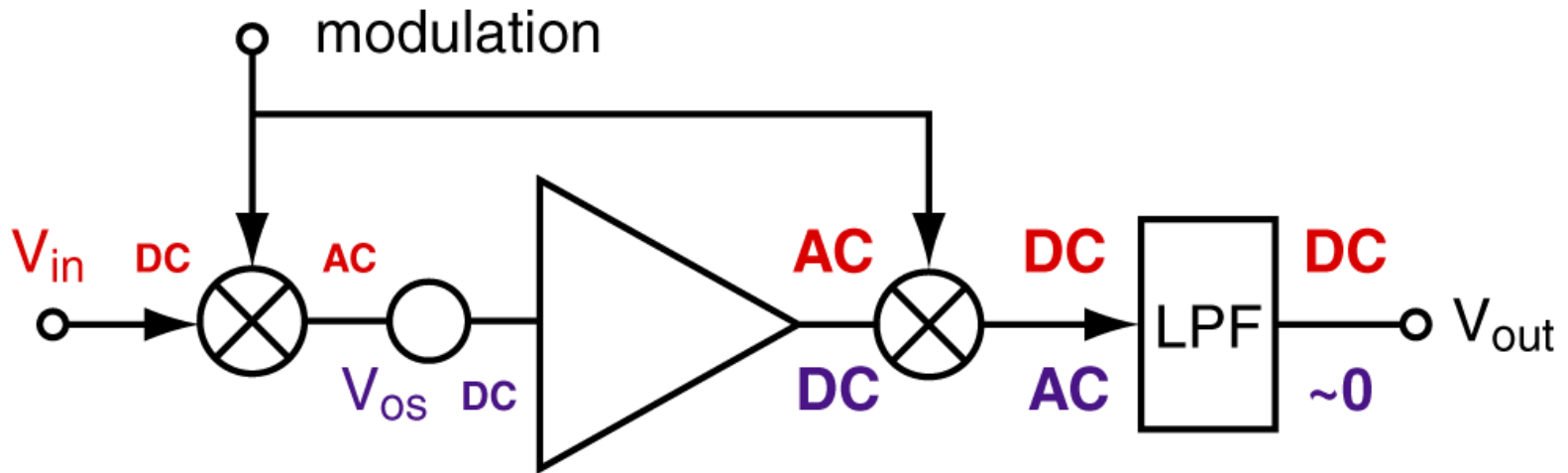

Signal is modulated, amplified and then demodulated again [9]

- + Output signal is continuously available
- Low-pass filter required


# Square-wave Modulation

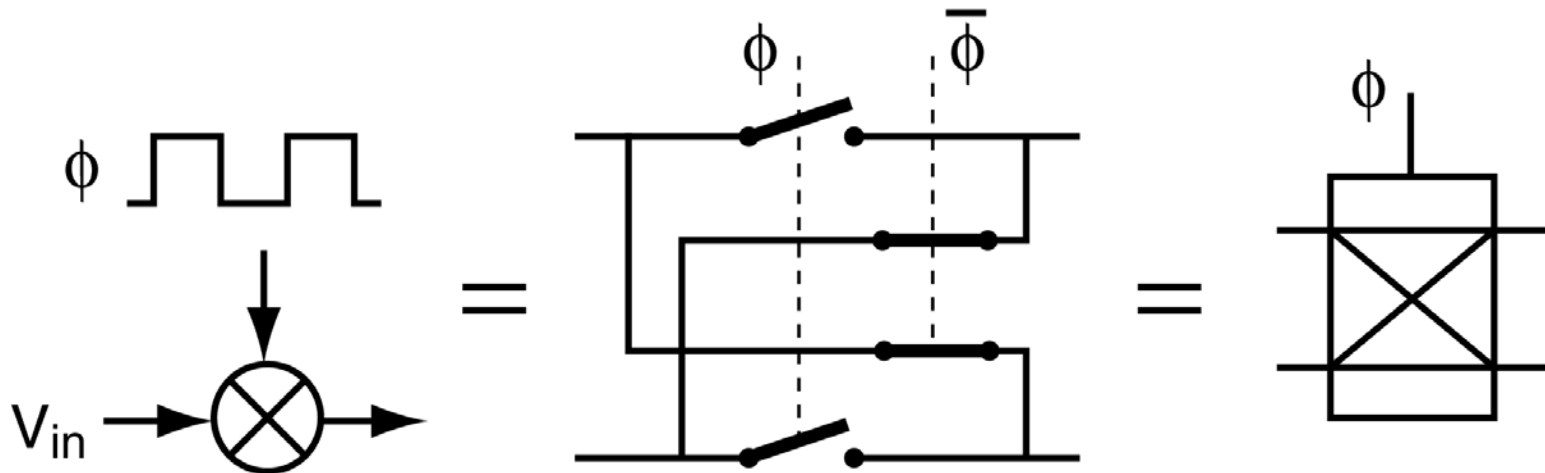


- Easily generated modulating signal
- The modulator is a polarity-reversing switch
- Switches are easily realized in CMOS



# Chopping in the Frequency Domain

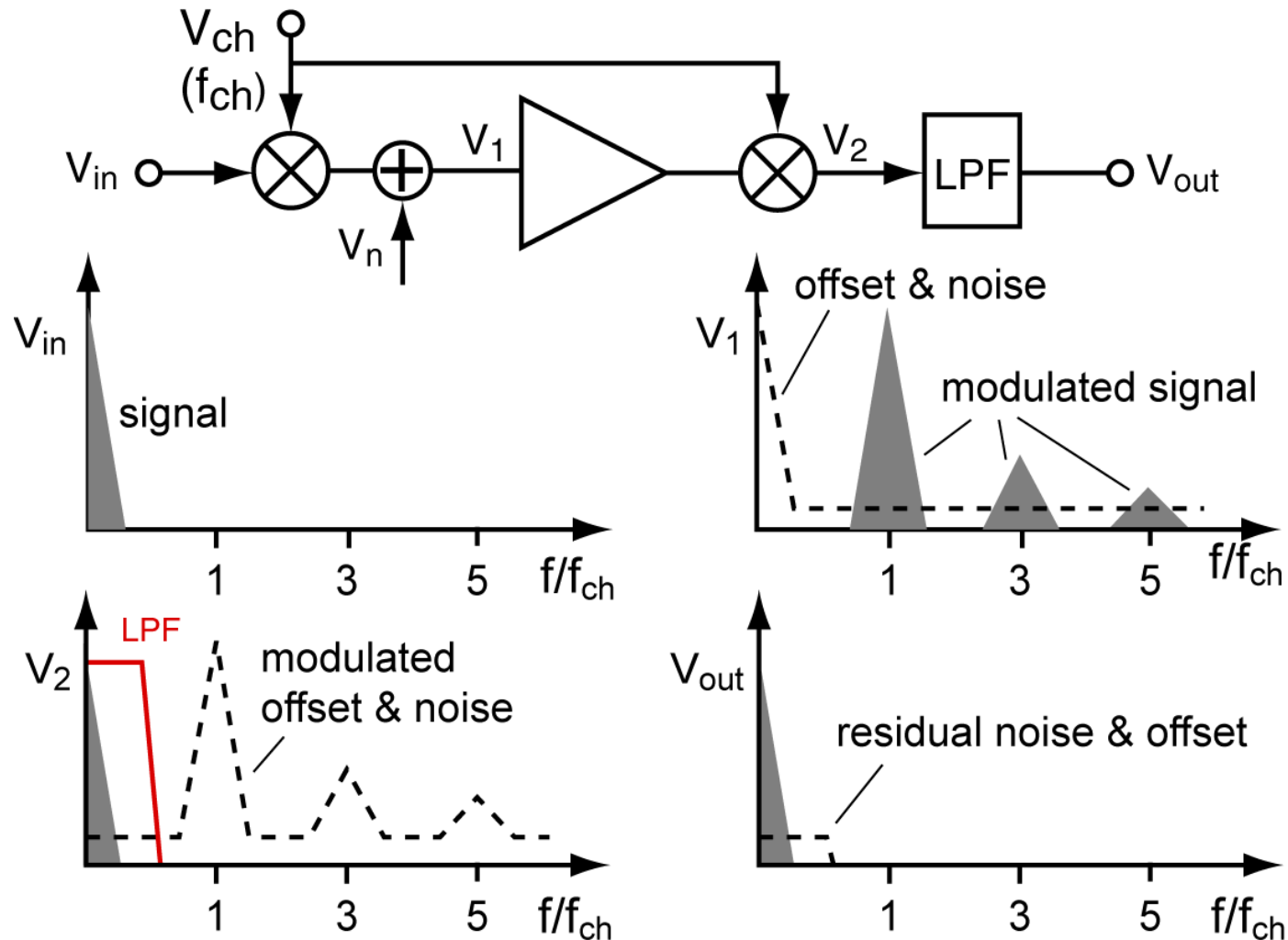


# Residual Noise of Chopping

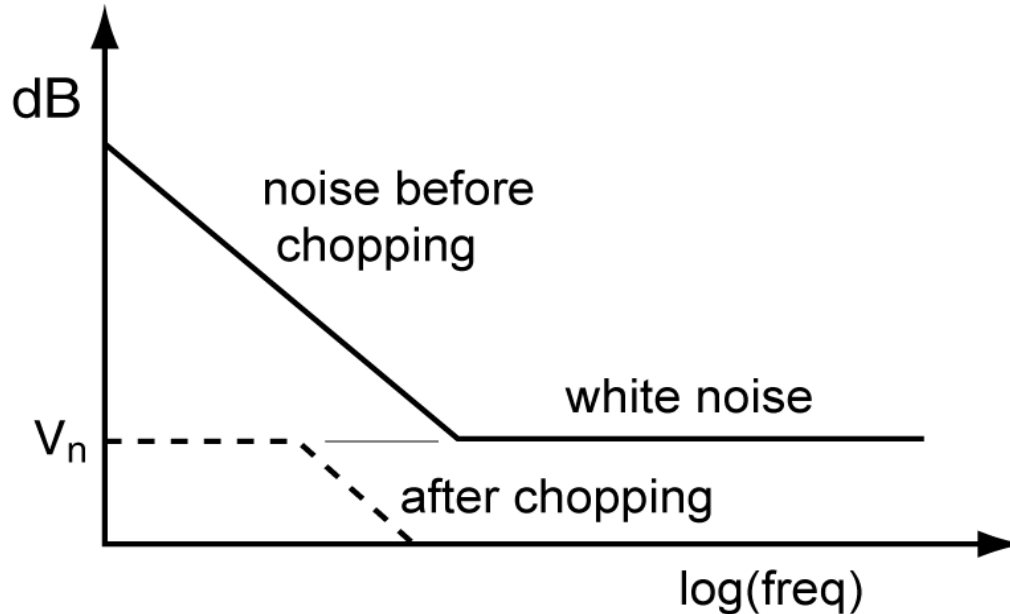


- $1/f$  noise is **completely** removed provided [6]  
 $f_{ch} > 1/f$  corner frequency
- Significantly better than auto-zeroing!
- State-of-the-art is  $8.5\text{nV}/\sqrt{\text{Hz}}$  [10]

# Chopping in the Time Domain

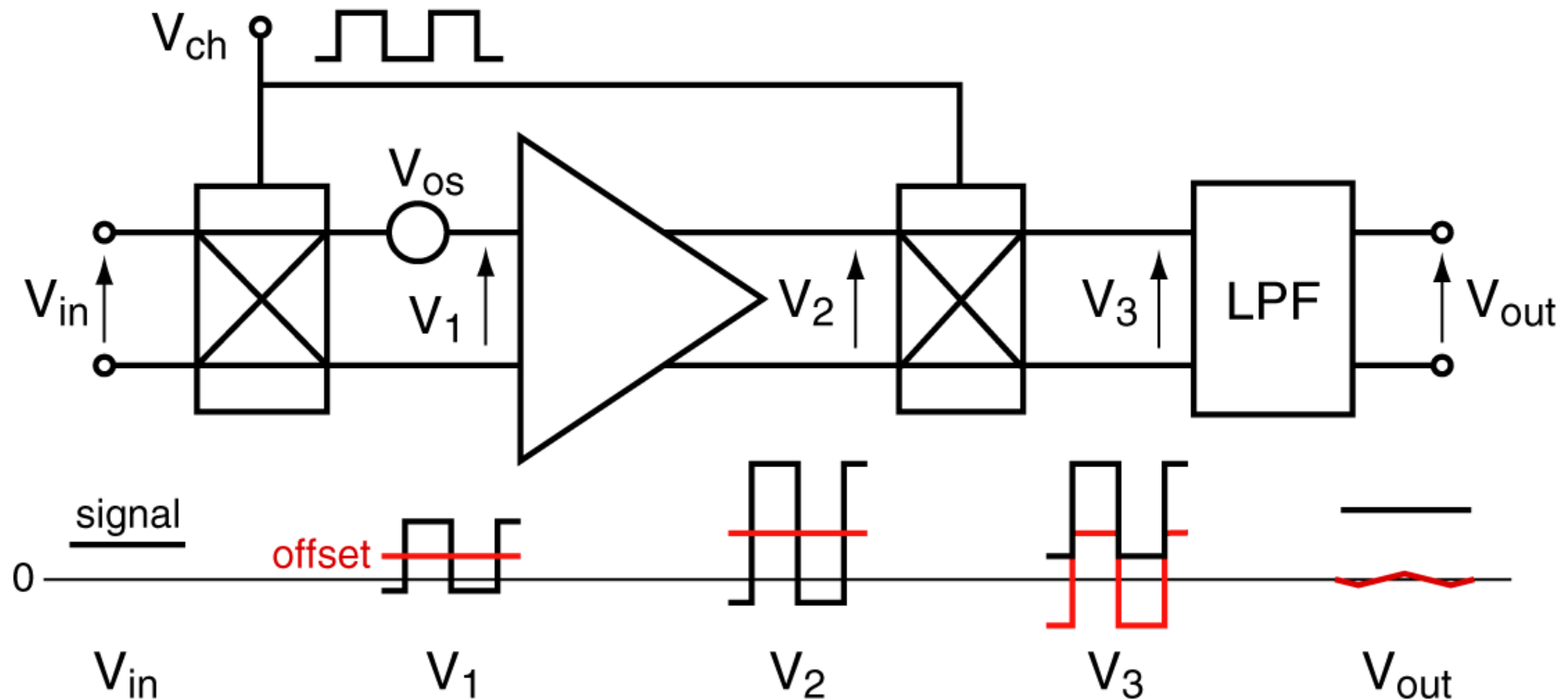


- Clock duty-cycle should be exactly 50%  $\Rightarrow \div 2$

# Bandwidth & Gain Accuracy

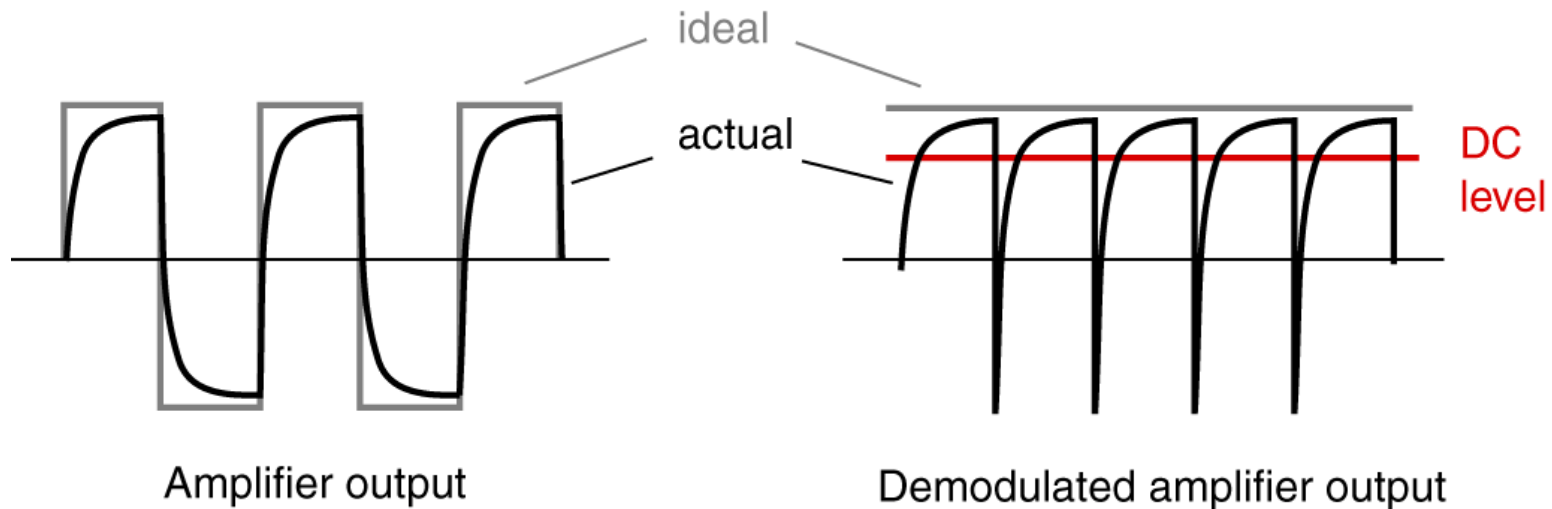


- Limited BW reduces effective gain
- $A_{\text{eff}} = A_{\text{nom}}(1 - 4\tau/T)$  for a 1<sup>st</sup> order LPF, where  $f_{\text{ch}} = 1/(2\pi\tau)$  and  $\tau \ll T$
- $T/\tau = 40 \Rightarrow 10\%$  error!

# Chopper Opamp

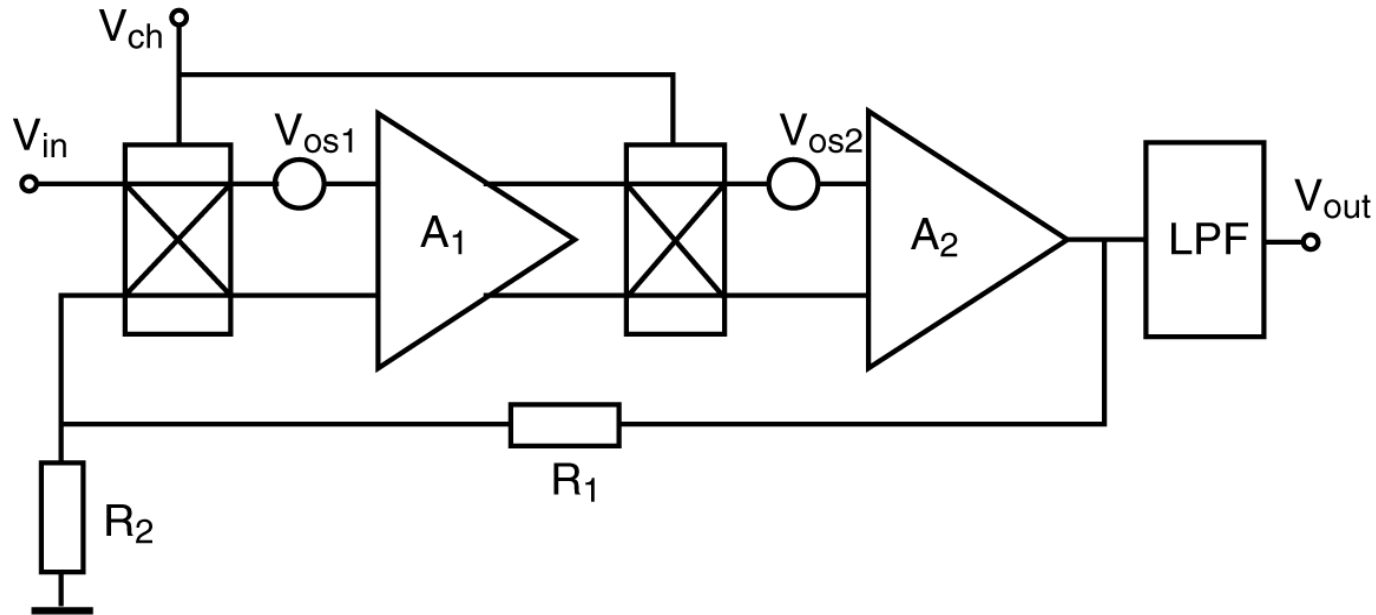


- Feedback resistors  $\Rightarrow$  Accurate gain [11,12]
- Offset is modulated, not the signal!
- To suppress  $V_{os2}$ ,  $A_1$  should have high gain

# Residual Offset of Chopping (1)

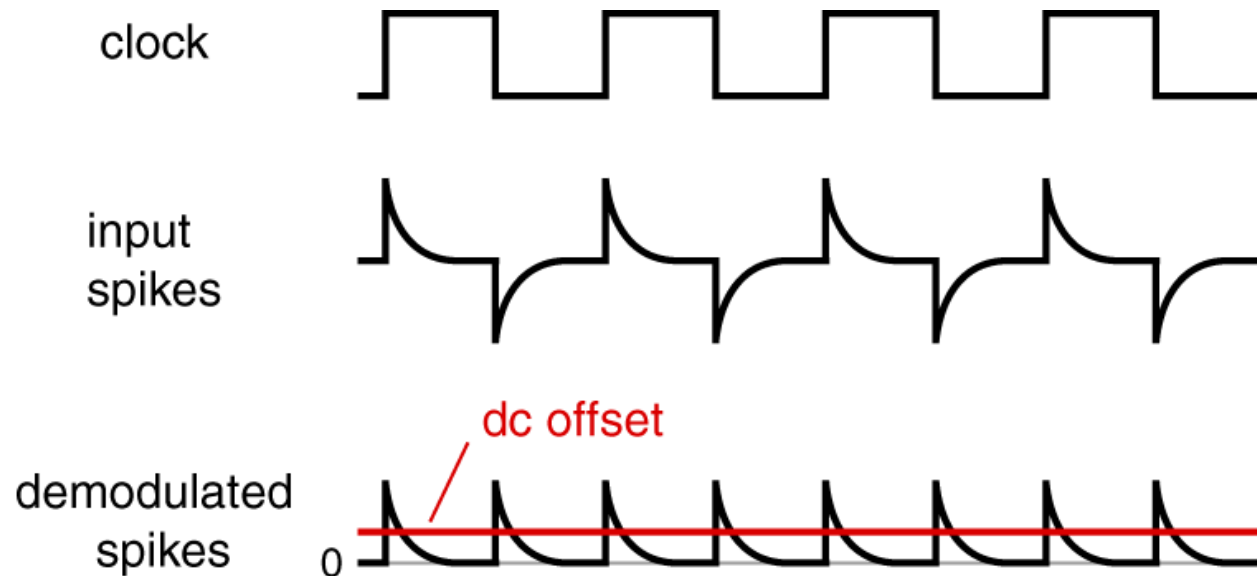


- Due to charge injection at the input chopper
- Causes a typical offset of a few  $\mu\text{V}$
- Input spikes  $\Rightarrow$  bias current (a few tens of pA)

# Residual Offset of Chopping (2)

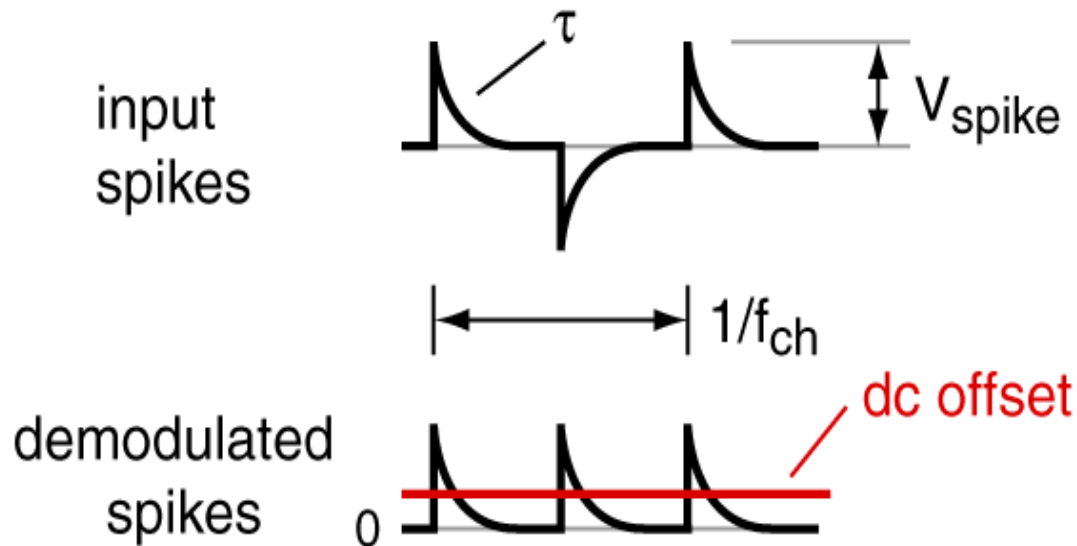

- Residual offset =  $2f_{\text{ch}} V_{\text{spike}} \tau$
- Linearly dependent on chopping frequency  $f_s$
- Spike time constant  $\tau$  will vary with source impedance


# Band-pass Filtering

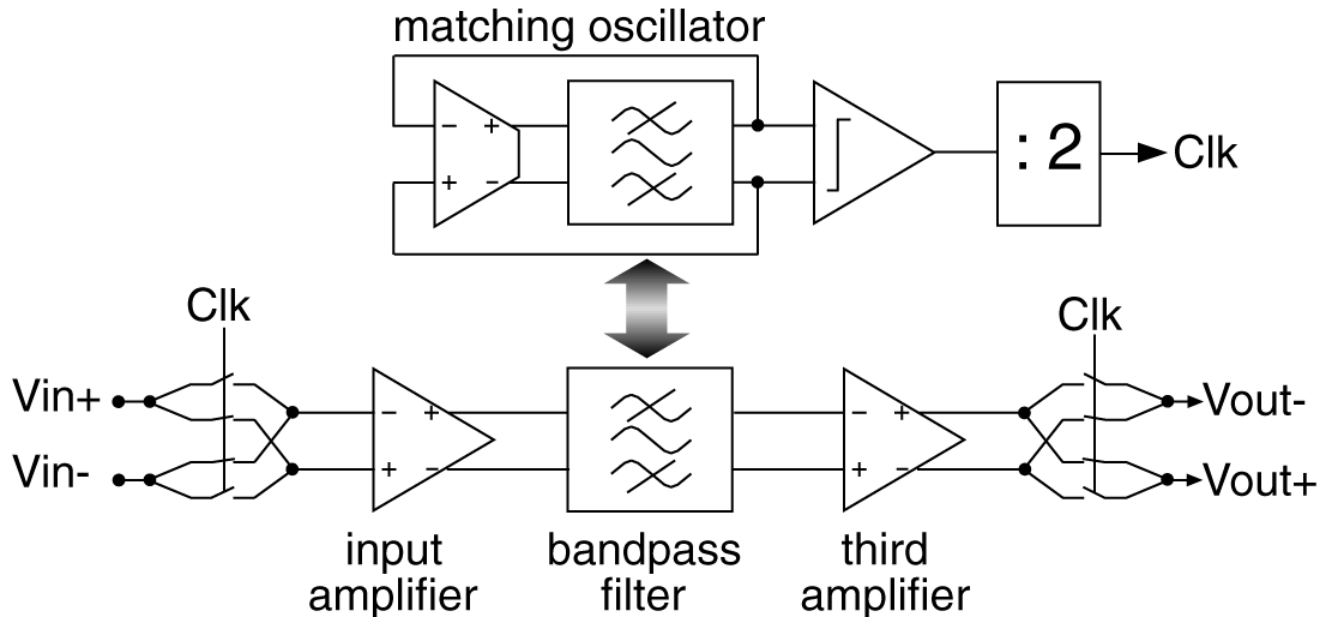

- BP (LP) filter reduces spike amplitude [10,13]
- Clock frequency tracks BP filter's center frequency  
⇒ low filter  $Q \sim 5$
- Residual offset  $< 1\mu\text{V}$ !




# Nested Chopper

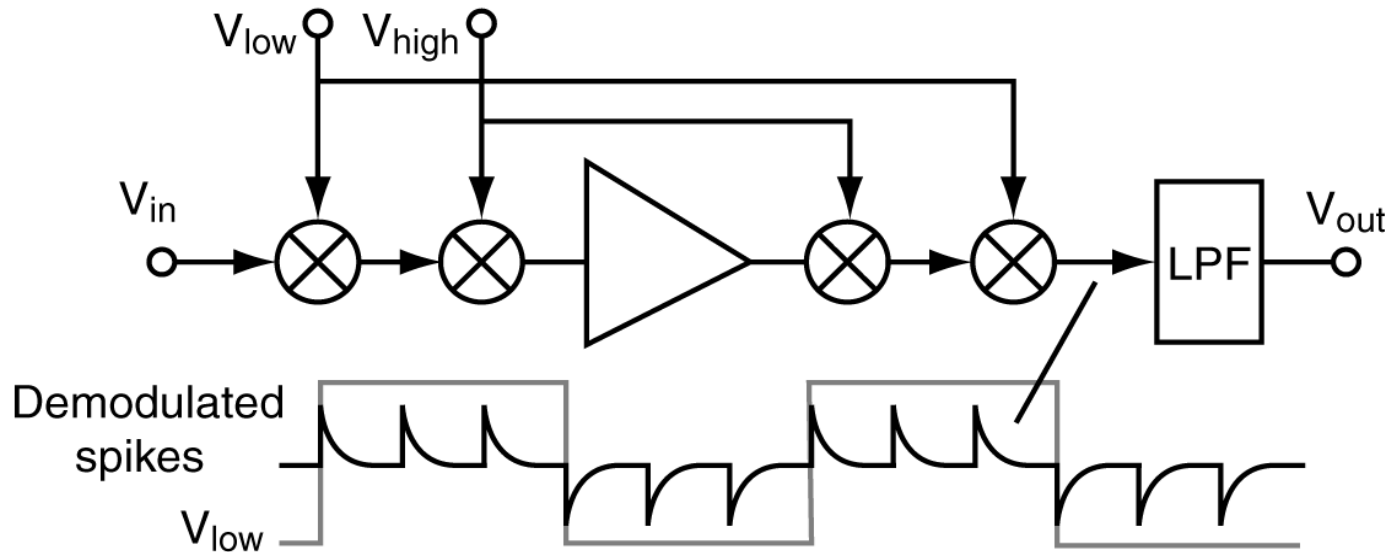



- Inner chopper removes  $1/f$  noise
- Outer chopper removes residual offset [11,14]
- Residual offset  $\sim 100\text{nV}$ !

# Chopper With Guard Band

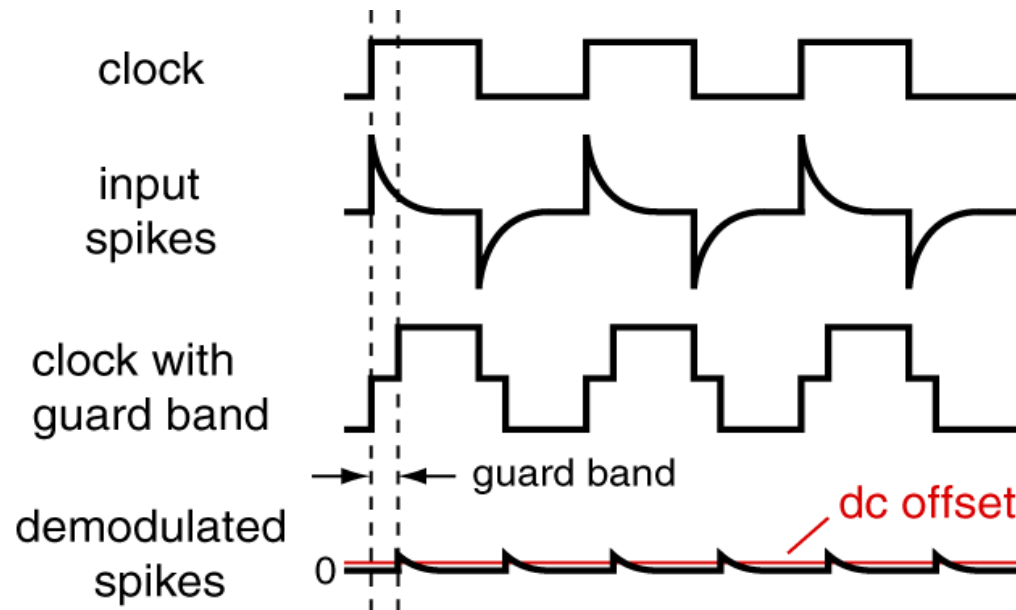



- During guard-band, output is shorted [15,16] or tri-stated [17]
- Residual offset  $\sim 200\text{nV}$ !
- Slightly worse noise performance

# Smart Thermal Wind Sensor

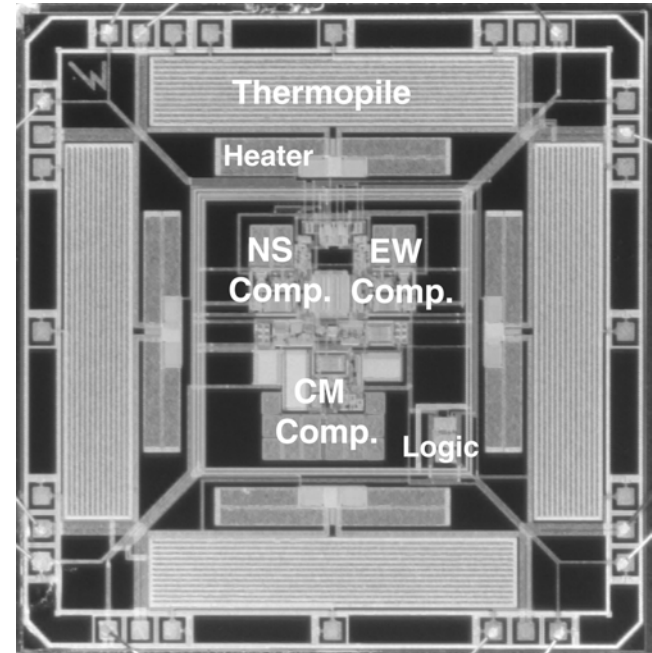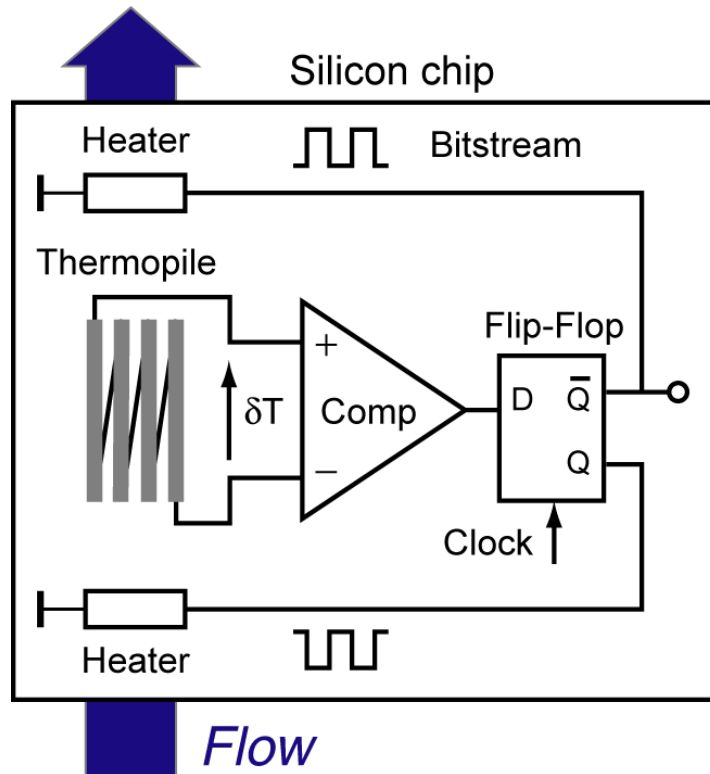



- Airflow induces a temperature gradient in chip
- Thermopiles are read-out by auto-zeroed comparators in a null-balance configuration [18]

# Smart Magnetic Field Sensor

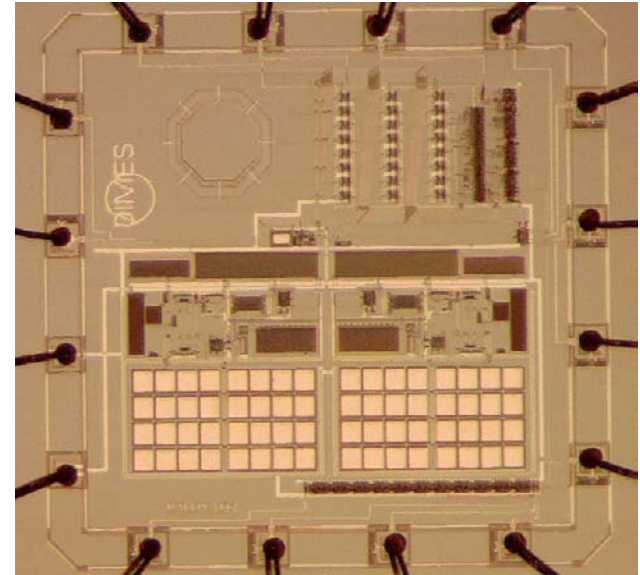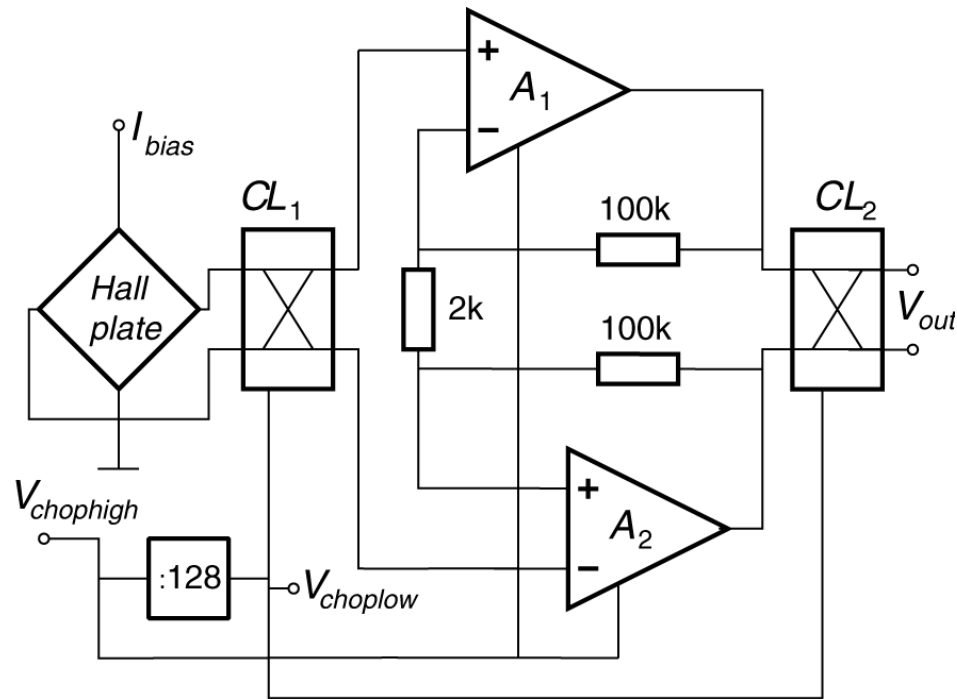


- Hall-plate is read-out using spinning-current & nested chopper techniques [19]
- Courtesy of A.Bakker, Philips Semiconductors, Delft

# Smart Temperature Sensor

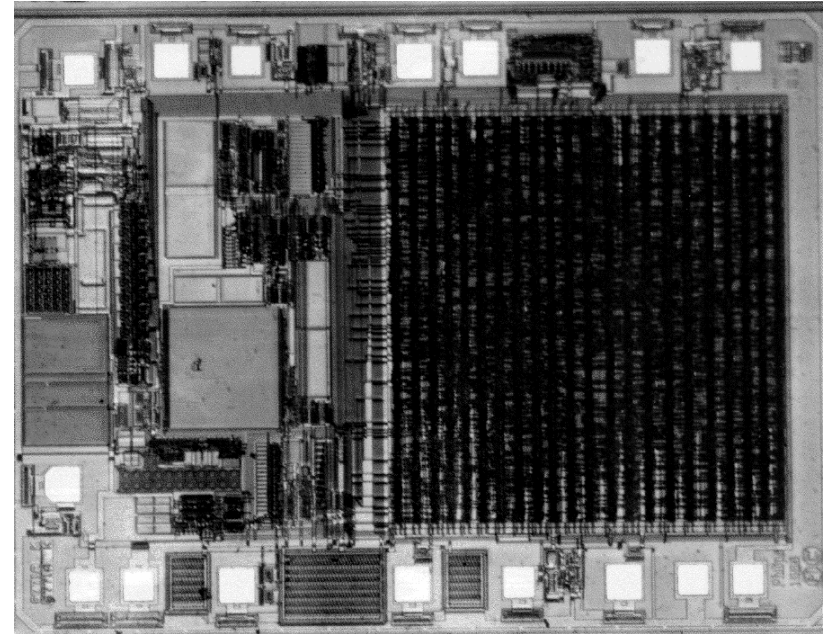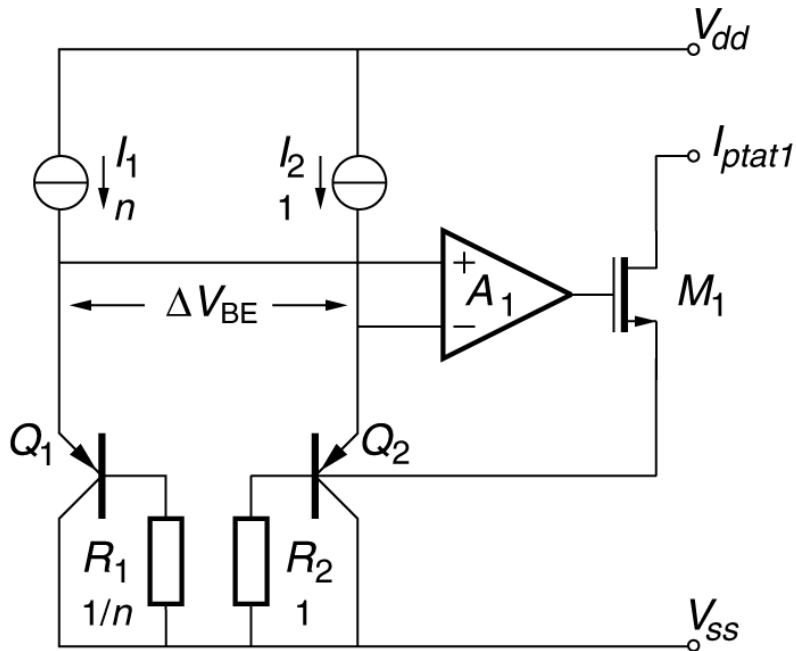


- $\Delta V_{be} \sim kT/q$  read-out using nested chopper technique  
 $\Rightarrow \pm 1^\circ\text{C}$  uncalibrated accuracy [14,20]
- Courtesy of A.Bakker, Philips Semiconductors, Delft

# Smart Calorimetric Gas Sensor

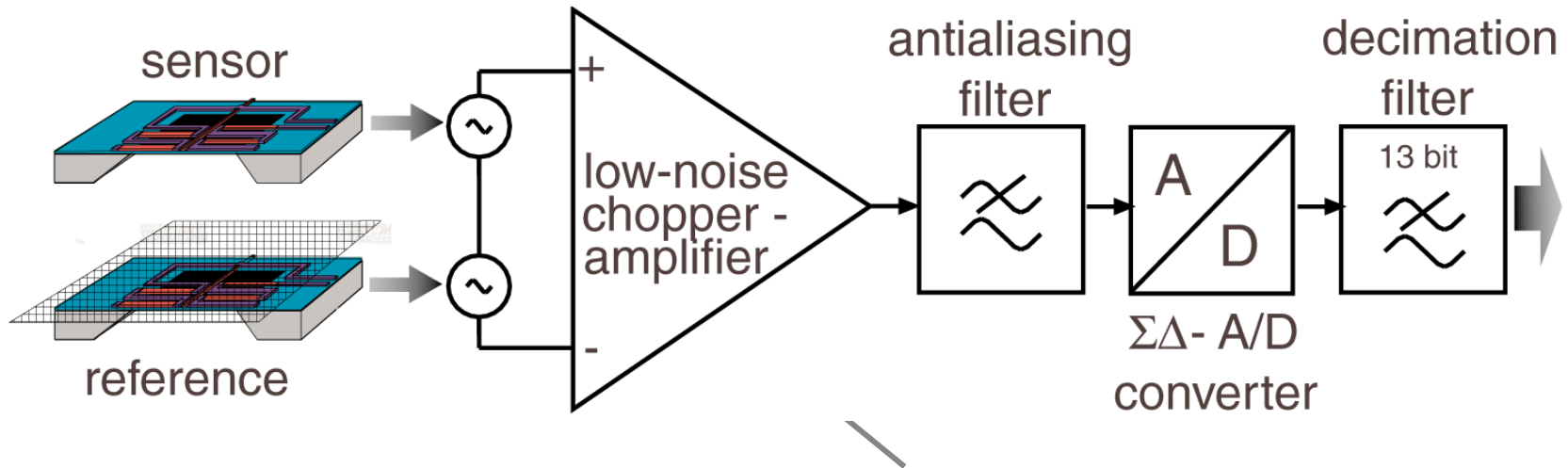

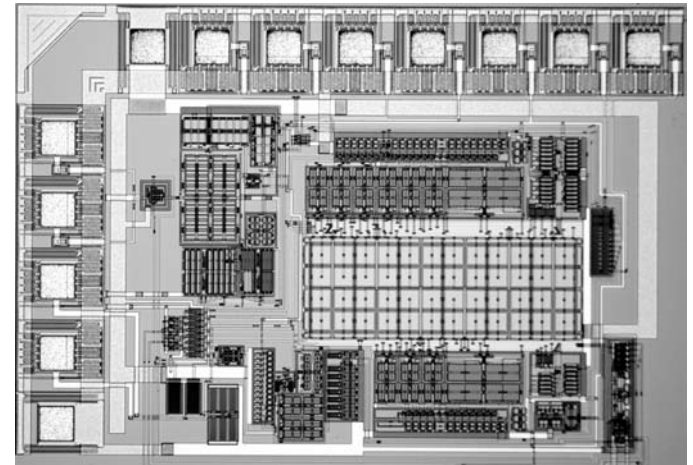- Calorimetric sensor read-out using BP chopper [21]
- Courtesy of C. Hagleitner, Physical Electronics Laboratory, ETH, Zurich



# Summary

- Mismatch and offset are part of life
- Trimming reduces offset but not the noise
- Auto-zeroing only reduces LF noise, but does not limit amplifier bandwidth
- Chopping eliminates LF noise, but limits amplifier bandwidth

# References (1)

1. P.R. Gray et al, "Analysis & Design of Analog Integrated Circuits," 4<sup>th</sup> edition, John Wiley & Sons, Inc., 2000.
2. A. Hastings, "The Art of Analog Layout," Prentice Hall, 2001.
3. G.A. Rincon-Mora, "Voltage references," IEEE Press, 2002.
4. C. Eichenburger, W. Guggenbuhl, "On charge injection in analog MOS switches and dummy switch compensation techniques," IEEE Trans. on Circuits & Systems, vol. 37, no. 2, Feb. 1990, p. 256-264.
5. C. Eichenberger, W. Guggenbuhl, "Charge injection of analogue CMOS switches," IEE Proc. G: Circuits, Devices & Systems, vol. 138, no. 2, April 1991, p.155-159.
6. C.C. Enz, G.C.Temes, "Circuit techniques for reducing the effects of op-amp imperfections: autozeroing, correlated double sampling and chopper stabilization," Proc. of the IEEE, vol. 84, no. 11, Nov. 1996, p. 1584 -1614.
7. Texas Instruments, TLC4501 data sheet, 1999.
8. Analog Devices Inc., AD8551 data sheet, 1999.



# References (2)

9. C.C. Enz et al., "A CMOS chopper amplifier," IEEE JSSC, vol.22, p.335-342, June 1987.
10. C. Menolfi, Q.Huang, "A fully integrated CMOS instrumentation amplifier with submicrovolt offset," IEEE JSSC, vol. 34, March 1999, p.415-420.
11. A. Bakker et al., "A CMOS nested chopper instrumentation amplifier with 100nV offset," IEEE JSSC, vol. 35, no. 12, 2000, p. 1877 - 1883.
12. K.A.A. Makinwa, J.H.Huijsing, "A wind sensor with an integrated low-offset instrumentation amplifier," Proc. of ICECS 2001, vol. 3, p. 1505-1508.
13. C. Menolfi, Q. Huang, "A low-noise CMOS instrumentation amplifier for thermoelectric infrared detectors," IEEE JSSC, vol. 32, no. 7, July 1997, p.968 - 976.
14. A. Bakker, "High-accuracy CMOS smart temperature sensors," Kluwer Academic Publishers, Boston, 2000.
15. C. Menolfi, Q.Huang, "A 200nV 6.5 nV/ $\sqrt{\text{Hz}}$  noise PSD 5.6kHz chopper instrumentation amplifier," Digest of ISSCC 2001, p. 362-363.

# References (3)

16. A. Bilotti, G. Monreal, "Chopper-stabilized amplifiers with a track-and-hold signal demodulator," IEEE Trans. On Circuits & Systems-I, vol. 46, April 1999, p. 490-495.
17. A. Thomsen, "DC measurement IC with 130nVpp noise in 10Hz, Digest of ISSCC 2000, p.334-335.
18. K.A.A. Makinwa, J.H.Huijsing, "A smart CMOS wind sensor," Digest of ISSCC 2002, p.432-433.
19. A. Bakker, J.H.Huijsing, "Low-offset, low-noise 3.5mW CMOS spinning-current Hall-effect sensor with integrated chopper amplifier," Proc. of Eurosensors XIII, Sept 1999, p.1045-1048.
20. C. Hagleitner et al., "N-well based CMOS calorimetric sensors," Proc. of MEMS 2000, p. 96-101.